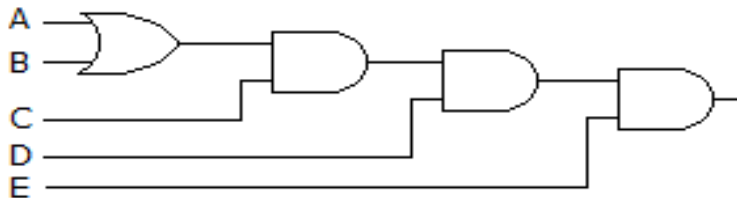


MEKDELA AMBA UNIVERSITY
DEPARTMENT OF COMPUTER SCIENCE

DIGITAL ELECTRONICS WORKSHEET

- Choose five questions as an assignment.
- Due date for assignment is date of your final exam
- Assignment weight: 25%

1. State and briefly explain advantages of digital circuits over analog circuits.
2. Convert the following binary numbers in decimal: **101110**; **1110101**; and **110110100**.
3. Convert the following decimal numbers to the bases indicated.
 - a. 7562 to octal
 - b. 1938 to hexadecimal
 - c. 175 to binary
4. Simplify the following expressions using Boolean algebra.
 - a. $AB + A(CD + CD')$
 - b. $(BC' + A'D)(AB' + CD')$
5. Determine the values of A, B, C, and D that make the sum term $A'+B+C'+D$ equal to zero.
6. Derive the Boolean expression for logic circuit shown below



7. Draw the logic diagram for the following Boolean expression.
 - A. $T_1 = XY + XZ + YZ$
 - B. $T_2 = Z'$

8. Simplify the Boolean expression $Z = (A'+B)(A+B)$.

9. Given the Boolean function $F = xy'z + x'y'z + xyz$

- a. List the truth table
- b. Draw the logic diagram of the original function using 2-input gates
- c. Simplify the function using Boolean algebra
- d. List the truth table of the simplified function
- e. Draw the logic diagram of the simplified function (using 2-input gates)
- f. Draw the logic diagram of the simplified function using only 2-input NAND gates

10. Discuss the difference between combinational and sequential digital circuits.

11. Discuss briefly the operations and applications of the following digital circuit building blocks.

- a) Multiplexers
- b) Decoders
- c) Registers
- d) Counters

12. Classify each of the following digital circuits as either a combinational circuit or a sequential circuit.

- a. Multiplexers
- b. Encoders
- c. Shift-registers

13. Design a logic circuit that has three inputs and whose output is high whenever two or more of the three inputs are low.

- I. Construct a 3-input truth table that meets the criteria given.
- II. Use the Karnaugh Map technique to find the reduced sum-of-product (SOP) expression.
- III. Draw the logic circuit for the reduced SOP expression.